

Numericals based on Module 4

1. Design an Astable Multivibrator using IC555 timer to generate an output waveform of 2kHz with 50% duty cycle.
2. Design a first order and second order Low pass filter circuit to have a cutoff frequency of 5 kHz using 741 op-amp.
3. Design a first order and second order High pass filter circuit to have a cutoff frequency of 2 kHz using 741 op-amp.
4. A second order low-pass filter has the following components: $R_1=68k\Omega$, $R_2=68k\Omega$, $R_3=150k\Omega$, $C_1=330pF$, $C_2=680pF$. Calculate the cutoff frequency.
5. A second order high-pass filter has the following components: $R_1=28k\Omega$, $R_2=56k\Omega$, $C_1=C_2=1300pF$. Calculate the cutoff frequency.
6. Design a single –stage bandpass filter to have a voltage gain of 1 and pass band from 1 kHz to 50 kHz.
7. A single stage band pass filter circuit has the following components: $R_1=R_2=R_3=3.9k\Omega$, $C_1=0.12\mu F$, $C_2=600pF$. Calculate its upper and lower cutoff frequencies.
8. Design a single stage band pass filter using 741 opamp with center frequency is to be 3.3 kHz and the pass band is to be approximately $\pm 50Hz$ on each side.